

# ECE311 FinalRC

Zong zihan  
2025.8.1





# Before we start...



## Reminders

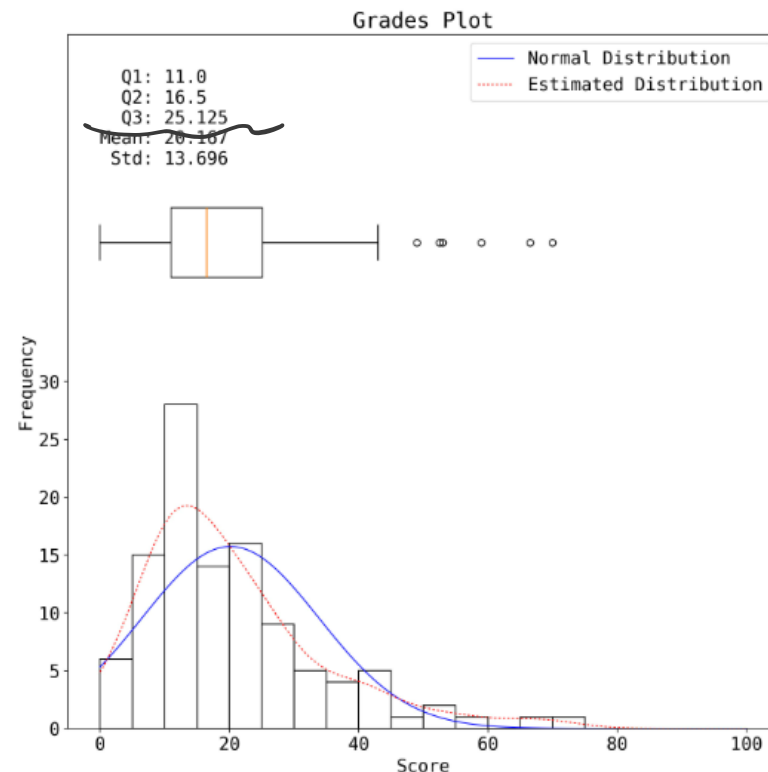1. Difficult exam!
2. Must go over all the questions!
3. Don't stick on one question!
4. More about understanding rather than calculating!



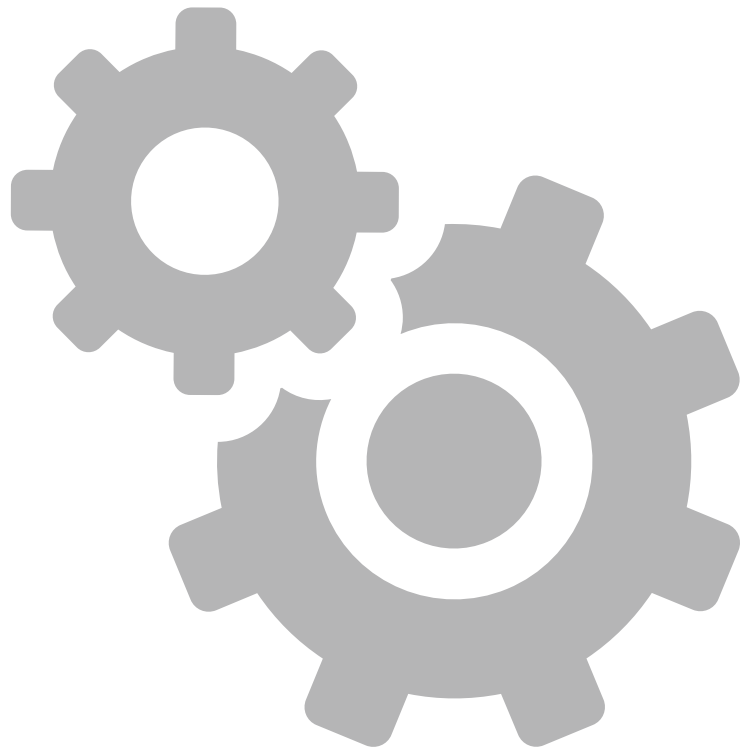

**1** Frequency Domain

**2** Bode Plot

**3** First Order Systems

**4** Parasitic Capacitance


**5** ~~Miller Effect~~

# Frequency Domain



## Definition Review


1. Transfer Function  $H(s)$

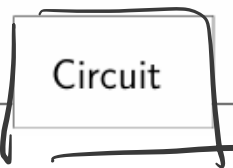$V_{in}(s)$  In —  Out —  $V_{out}(s)$

$H(s) = \frac{V_{out}}{V_{in}}$

2. Use S-domain to Get Time Response



3. Partial Fraction Expansion

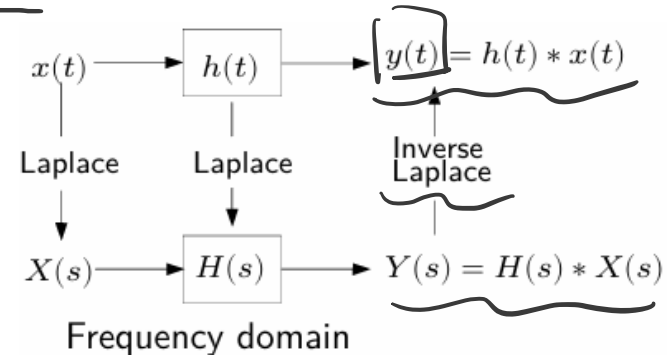



## Definition Review

### Capacitors and Inductors

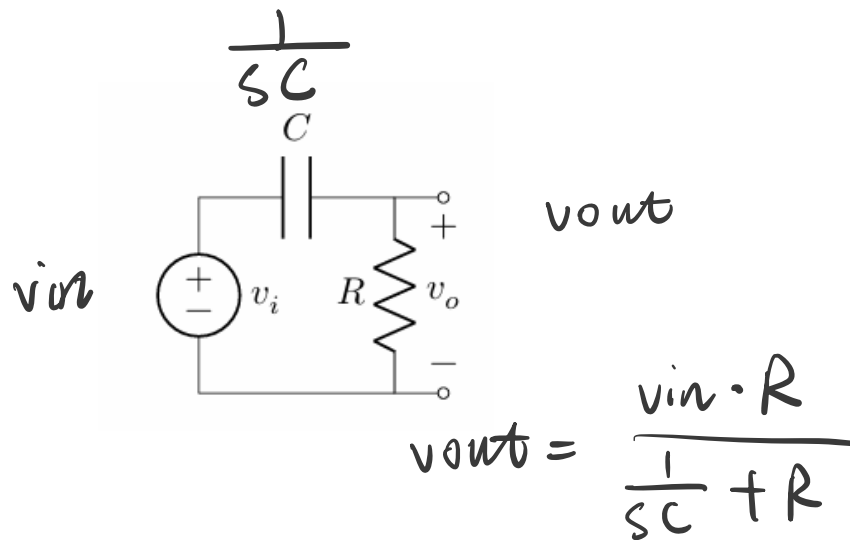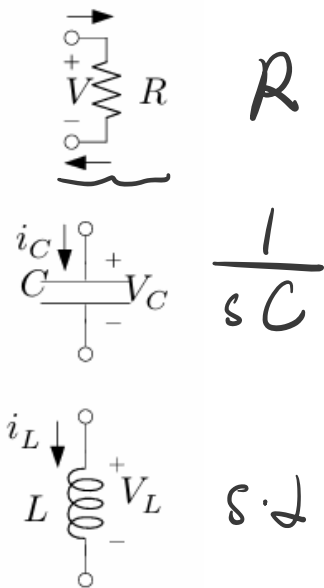

# Frequency Domain




## Pole and Zero

$$|H(s_z)| = 0 \xrightarrow{s} H(s) = 0$$

$$G(s) = \frac{s+2}{s^2+5s}$$

$$G(s) = \frac{s+2}{s \cdot (s+5)}$$

$$|H(s_p)| = \infty$$

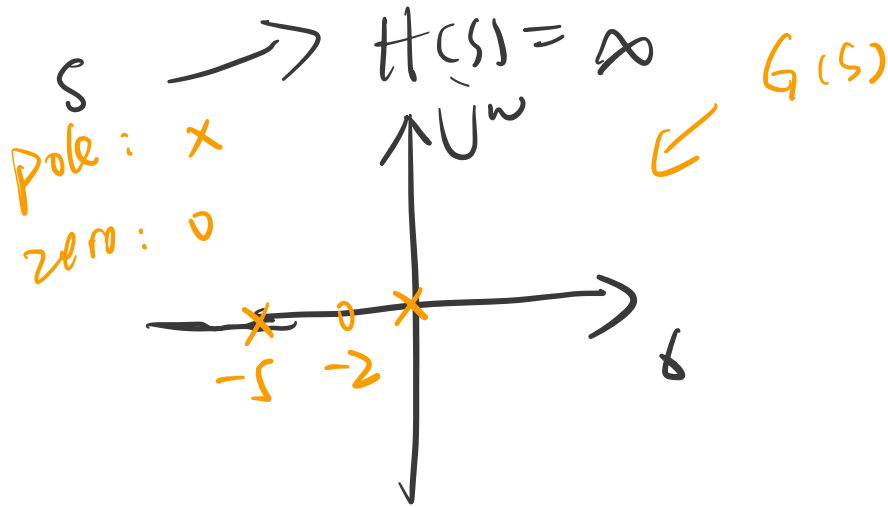

pole: 0 and -5

zero: -2

# Frequency Domain



## Get Diff. Eq from $H(s)$

$$H(s) = 3 \frac{(s+4)}{s^2 + 2s + 5} \rightarrow \frac{Y(s)}{X(s)}$$

$$s^n X(s) \xrightarrow{\text{Time domain}} \frac{d^n X(t)}{dt^n}$$

$$(s^2 + 2s + 5) \cdot Y(s) = 3(s+4) \cdot X(s)$$

$$\frac{d^2 y(t)}{dt^2} + 2 \cdot \frac{dy(t)}{dt} + y(t) = 3 \frac{dx(t)}{dt} + 12 x(t)$$

# Frequency Domain



## Magnitude and Phase


$$|H(s)| = K \frac{\prod_{i=1}^m |s - z_i|}{\prod_{i=1}^n |s - p_i|}$$

$$\angle H(s) = \sum_{i=1}^m \angle(s - z_i) - \sum_{i=1}^n \angle(s - p_i)$$

$$|H(s)| = K \frac{r_1 \dots r_m}{q_1 \dots q_n}$$

$$\angle H(s) = (\phi_1 + \dots + \phi_m) - (\theta_1 + \dots + \theta_n)$$

$$H(s) = K \cdot \frac{\prod_{i=1}^m |s - z_i|}{\prod_{i=1}^n |s - p_i|}$$

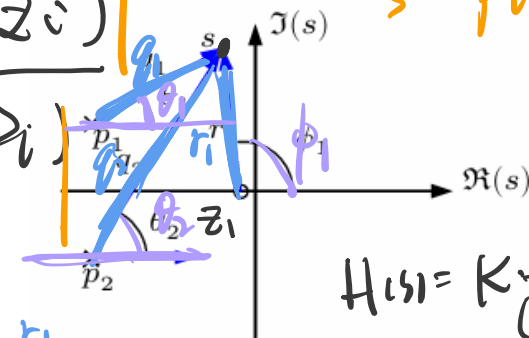

$$|H(s)| = K \cdot \frac{r_1}{q_1 \cdot q_2}$$

$$\angle H(s) = \phi_1 - \theta_1 - \theta_2$$

$$H(s) = K \cdot \frac{(s - z_1)}{(s - p_1)(s - p_2)}$$

$p_1, p_2 \dots$




# Bode Plot




## Construction Example

pair of complex pole

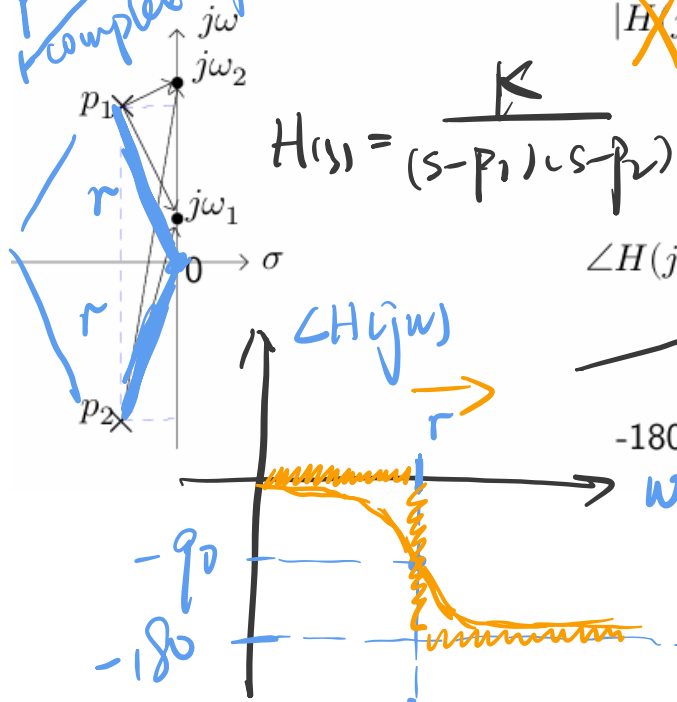

$20 \log_{10} |H(j\omega)|$  dB  
if pole is complex  
-40 dB -180°

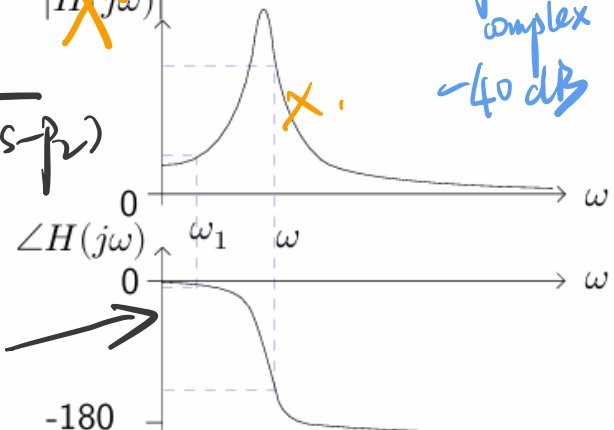

Pole (left plane)

- For lefthand plane
  - Slope changes by -20 dB/decade
  - Phase decreases by 90°

Zero

- Slope changes by 20 dB/decade
- Phase increase by 90°

right plane

slope 20 dB  
increase 90°  
slope -20 dB  
decrease 90°

# 

## 

$$H(j\omega) = \frac{1}{j\omega + 1}$$

$$H(s) = s$$

$$H(s) = \frac{1}{s} \text{ and } s = j\omega$$

$$H(s) = \frac{1}{(1 + \frac{s}{10})(1 + \frac{s}{10^4})}$$





$$H(s) = \frac{1}{s+1}$$

$$= |A_0| \angle H(s)$$

for zero for pole


in left plane

$$|A_0| = 1$$

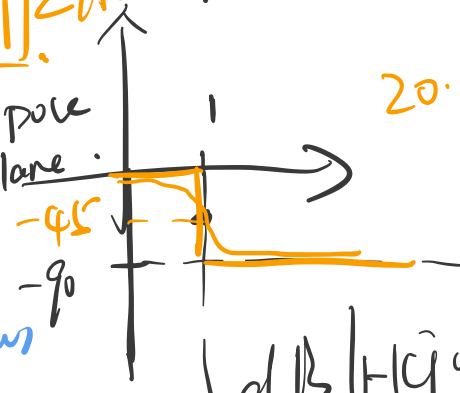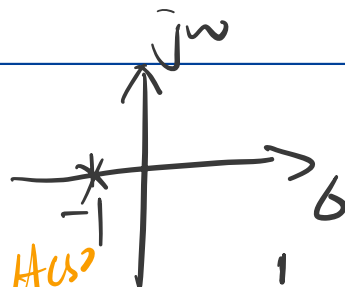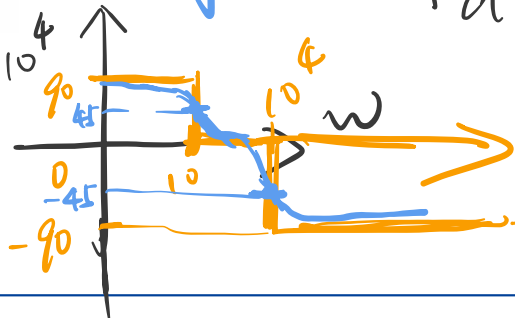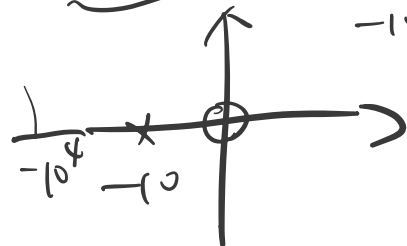

$$H(s) = A_0 \frac{(1 - \tau_1 s) \dots (1 - \tau_n s)}{(1 - \tau_{n+1} s) \dots (1 - \tau_{m+1} s)}$$

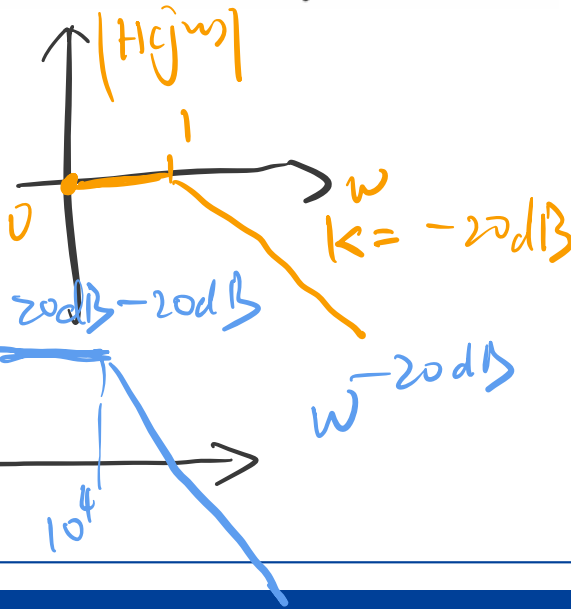
- For lefthand plane
  - Slope changes by -20 dB/decade
  - Phase decreases by 90°
- Zero
  - Slope changes by 20 dB/decade
  - Phase increase by 90°



# Bode Plot



## Bandwidth and Gain-Bandwidth Product

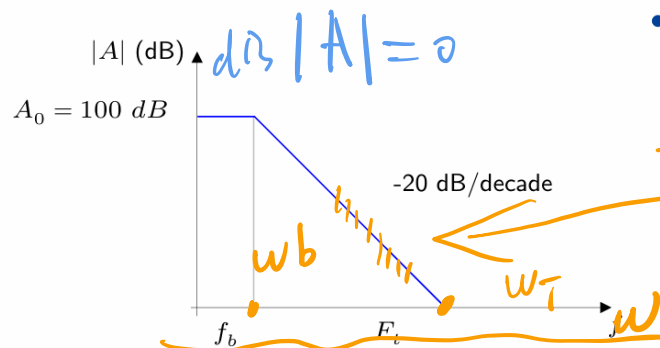

- $f(t)$  ( $\omega_t$ ) is  $\omega$  where  $|A(j\omega)| = 1$

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_b} \quad (24)$$

$$1 \approx \frac{A_0}{\omega_T/\omega_b} \Rightarrow \omega_T \approx A_0 \omega_b \quad (25)$$

$$\omega_T \approx A_0 \omega_b \quad (26)$$

- For lefthand plane
  - Slope changes by  $-20$  dB/decade
  - Phase decreases by  $90^\circ$
- Zero
  - Slope changes by  $20$  dB/decade
  - Phase increase by  $90^\circ$

### Recommendations for GBW calculation:

Draw the magnitude plot in dB directly to solve for bandwidth!

Or derive the equation and set it to 1

Both are OK!

Typically only one solution is needed to be considered!

$$\frac{s^2}{w_b^2} = 1 \rightarrow \boxed{s = w_b \cdot}$$

$$\begin{aligned} |A_0 \omega_b| & \quad (26) \quad |A_0 \hat{y}_\omega| = \frac{|A_0|}{\sqrt{2}} \\ \left| \frac{A_0}{1 + \frac{s}{\omega_b}} \right| &= \left| \frac{A_0}{\sqrt{2}} \right| = \frac{1}{\sqrt{2}} \downarrow \\ \rightarrow \frac{1}{(1 + \frac{j s}{\omega_b})(1 - \frac{j s}{\omega_b})} &= \frac{1}{1 + \frac{s^2}{\omega_b^2}} = \frac{1}{\sqrt{2}} \end{aligned}$$

# Bode Plot



## Bandwidth and Gain-Bandwidth Product

$$V_{out}(\omega) = A(\omega)V_{Id} = A(\omega)(V_{in} - V_n) \quad V_{out} = \frac{A_0}{1 + \frac{s}{\omega_b}} (V_{in} - \beta V_{out})$$

$$V_{out} = A(\omega)(V_{in} - \beta V_{out})$$

$$V_{out} \cdot \left(1 + \frac{A_0\beta}{1 + \frac{s}{\omega_b}}\right) = \frac{A_0}{1 + \frac{s}{\omega_b}} V_{in}$$

1-pole-zero plot

2. mag Bode plot

3. phase Bode plot

4 bandwidth

5. GBP

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{s}{\omega_b}} \cdot \frac{1}{\frac{A_0\beta}{1 + \frac{s}{\omega_b}} + 1}$$

$$= \frac{A_0'}{1 + \frac{s}{\omega_b}}$$

# First Order Systems



## Definition

Contains 1 pole and at most 1 zero

$$H(S) = \frac{a_0 + a_1 S}{1 + bS}$$

$$H(s) = \frac{H^0 + H^1 \tau s}{1 + \tau s}$$

$$\tau = RC_1$$

$$\tau = \frac{L_1}{R_0}$$

To find the time constant, remove the cap/ind nulling all the sources, find the resistance.

independent source.

To find transfer constant  $H^0$ , it is just the low frequency gain.

cap  $\rightarrow$  open circuit

ind  $\rightarrow$  short circuit

To find the transfer constant  $H^1$ , we look into high frequency response, so the cap shall be shorted. For inductor it is the opposite.


cap  $\rightarrow$  short

ind  $\rightarrow$  open

# First Order Systems



## Example

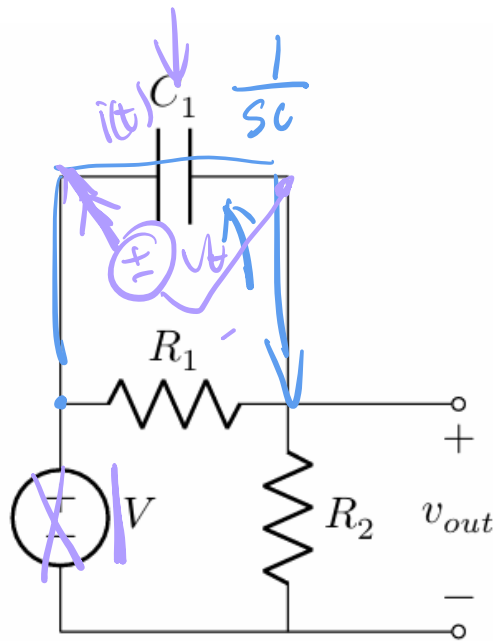

$$H(s) = \frac{H^0 + H^1 \tau s}{1 + \tau s}$$

216/215

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{R_2}{\left(\frac{1}{sC} \parallel R_1\right) + R_2}$$

311:

$$H^0 = \frac{v_{out}}{v_{in}} = \frac{R_2}{R_2 + R_1}$$

$$H^1 = \frac{v_{out}}{v_{in}} = 1$$

$$\tau = R \cdot C$$


$$R = R_1 \parallel R_2$$

$$H(s) = \frac{R_2}{R_1 + R_2} + \frac{(R_1 \parallel R_2) C s}{1 + (R_1 \parallel R_2) C s}$$

# First Order Systems




## Example

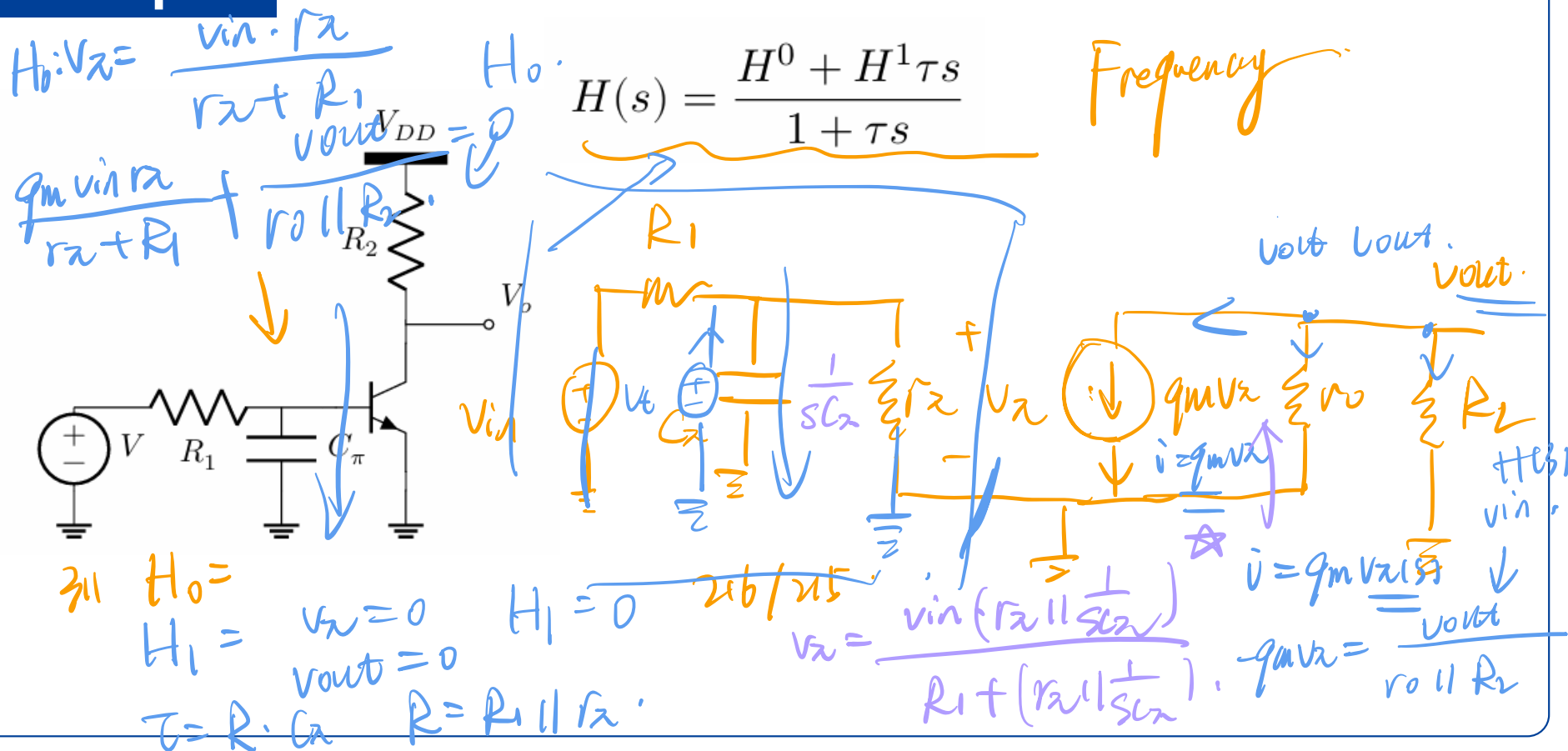
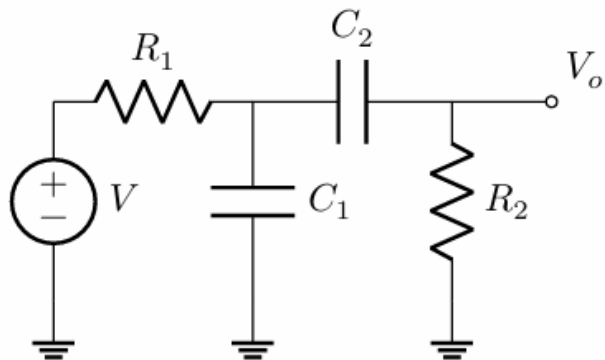
## Example

$$H(s) = \frac{a_0 + a_1 S + a_2 S^2 + \dots}{1 + b_1 S + b_2 S^2 + \dots}$$



Too hard for me to explain it explicitly... (For myself I can not understand what prof is talking about...)

Too many parameters

Suggest ECE216 methods for analyzing and work out the parameter conversely

**Tips:** the voltage and current relationship in frequency domain still holds!





## Bandwidth Estimation

$$H(s) \approx \frac{a_0}{1 + b_1 s + b_2 s^2 + \dots + b_n s^n}$$

$$H(s) \approx \frac{a_0}{1 + b_1 s}$$

$$\omega_h \approx \frac{1}{b_1} = \frac{1}{\sum_{i=1}^N \tau_i^0}$$

# Parasitic Capacitance



## Definition


Triode

$$C_{GS} = W_{ov} + \underbrace{1/2 (WLC_{ox})} \quad (1)$$

$$C_{SB} = \underbrace{WEC_j + 2(W + E)C_{jsw}} \quad (3)$$

$$C_{GD} = WC_{ov} + \underbrace{1/2 (WLC_{ox})} \quad (2)$$
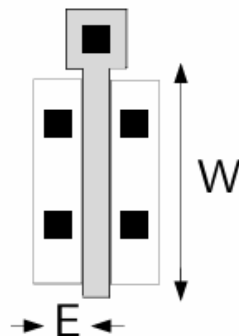
$$C_{DB} = \underbrace{WEC_j + 2(W + E)C_{jsw}} \quad (4)$$



Saturation

$$C_{GS} = WC_{ov} + \underbrace{2/3 (WLC_{ox})} \quad (5)$$

$$C_{SB} = \underbrace{WC_j + 2(W + E)C_{jsw}} \quad (7)$$

$$C_{GD} = \underbrace{WC_{ov}} \quad (6)$$

$$C_{DB} = \underbrace{WEC_j + 2(W + E)C_{jsw}} \quad (8)$$

# Parasitic Capacitance



## Parameter

$$\epsilon_{ox} = 3.9 \epsilon_0 \quad \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

NMOS Model

LEVEL = 1

NSUB =  $9e + 14$

TOX =  $9e - 9$

MJ = 0.45

VTO = 0.7

LD =  $0.08e - 6$

PB = 0.9

MJSW = 0.2

GAMMA = 0.45

UO = 350

CJ =  $0.56e - 3$

CGDO =  $0.4e - 9$

PHI = 0.9

LAMBDA = 0.1

CJSW =  $0.35e - 11$

JS =  $1.0e - 8$

PMOS Model

LEVEL = 1

NSUB =  $5e + 14$

TOX =  $9e - 9$

MJ = 0.5

VTO = -0.8

LD =  $0.09e - 6$

PB = 0.9

MJSW = 0.3

GAMMA = 0.4

UO = 100

CJ =  $0.94e - 3$

CGDO =  $0.3e - 9$

PHI = 0.8

LAMBDA = 0.2

CJSW =  $0.32e - 11$

JS =  $0.5e - 8$



# Parasitic Capacitance



## Example




NMOS

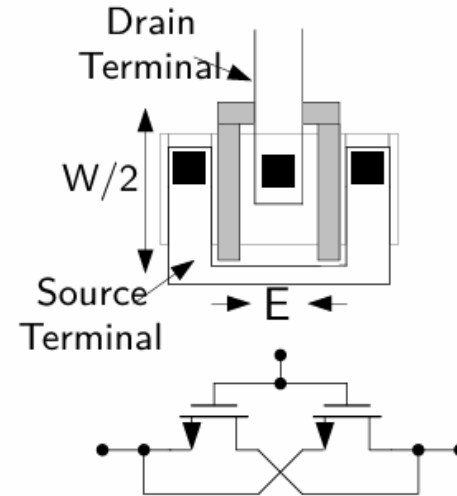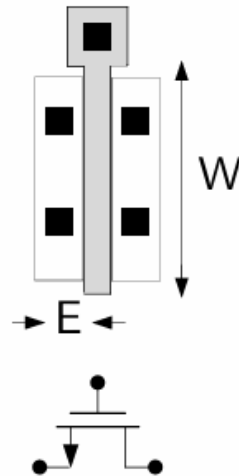


# Miller Effect

## Definition

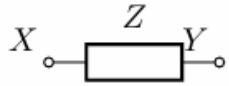

$$Z_1 = \frac{Z}{1 - A_v} \quad (31)$$

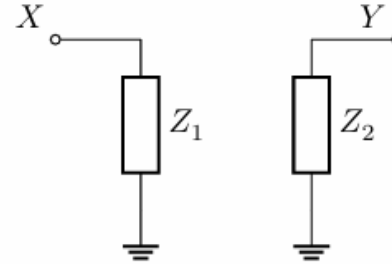



$$Z_2 = \frac{Z}{1 - \frac{1}{A_v}}$$

Note: There must be another way between X and Y

# Miller Effect



## Example

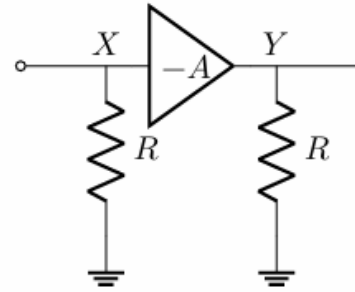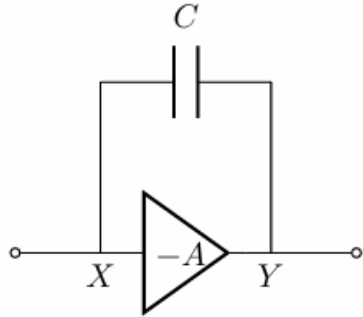

$$Z_1 = \frac{\frac{1}{SC_F}}{1 + A} = \frac{1}{S(1 + A)C_F}$$

$$Z_2 = \frac{\frac{1}{SC_F}}{1 + \frac{1}{A}} = \frac{1}{S\left(1 + \frac{1}{A}\right)C_F}$$

# Miller Effect



## Example

Output impedance

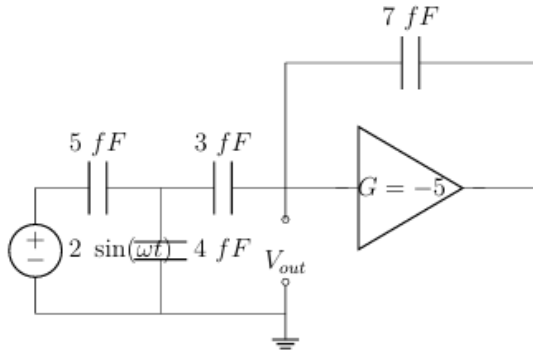


Figure 2: Miller



# Thanks!

