

ECE3110J Electronic Circuit Homework 5

Due: Jul 1st 11:59 a.m.

Note.

- 1) Please use A4 size paper or page.
- 2) Please clearly state your final result for each question.
- 3) For questions asking for *plot*, you can either sketch or use computer software (Matlab, Python). But make sure to mark all the important values on the graph.

Christina, a talented young engineer, has recently joined Blue Tiger Electronics. Christina's demanding supervisor, Xuyang, is determined to outshine their rival company, Red Tiger Technologies, and secure a prestigious government contract that will ensure Blue Tiger's dominance in the industry. To achieve this, Xuyang assigns Christina a series of challenging tasks to demonstrate Blue Tiger's superior MOSFET technology.

Question 1. Saturation of the $I - V$ Characteristics

Xuyang shows a datasheet of an NMOS transistor but there is only one figure on it, as Fig. 1 shows. Christina knows that for any semiconductor component, one of the most important things is to learn the $I - V$ characteristics.

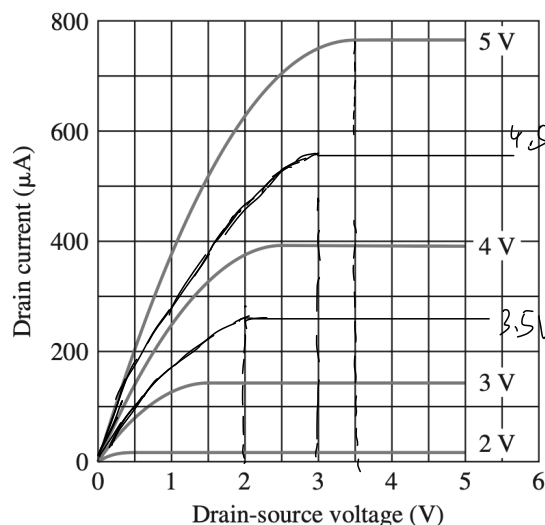


FIGURE 1. $I - V$ curves

- (1) She first determines the values of V_{TH} and k_n of this NMOS transistor.
- (2) Then, she adds the $V_{GS} = 3.5V$ and $V_{GS} = 4.5V$ curves to Fig. 1.

(1) $V_{TH} = V_{GS} - V_{DS} = 5V - 3.5V = 1.5V$. $k_n = \mu_n C_{ox} \frac{W}{L}$

$I_D = \frac{1}{2} k_n (V_{GS} - V_{TH})^2$ $\frac{1}{2} \cdot 2 \cdot 5^2 \cdot k_n = 3.5 \times 10^{-6}$

$k_n = 1.26 \times 10^{-4}$

Question 2. MOSFET DC Analysis I

Next, Xuyang assigns Christina the task of analyzing several simple circuits involving the MOSFET. For the circuits in Fig. 2, $V_{DD} = 3V$, $V_{TH} = 0.7V$ for NMOS, $V_{TH} = -0.8V$ for PMOS. She needs to sketch V_{out} as a function of V_{in} for each circuit as V_{in} varies from 0 to V_{DD} . Ignore body effect and channel length modulation.

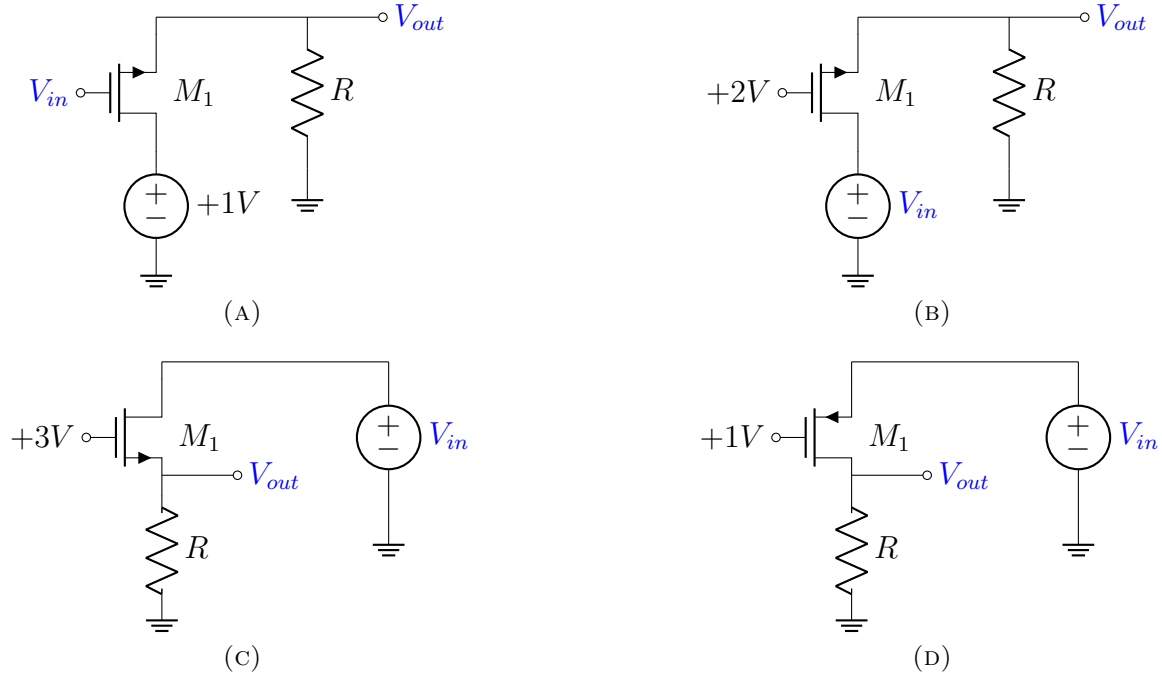


FIGURE 2. MOSFET circuits

Question 3. MOSFET DC Analysis II

Then, Xuyang assigns Christina the task of finding DC bias current I_D through the NMOS transistor in Fig. 3. $V_{TH} = 1V$, $\lambda = 0$, $k_n = \mu_n C_{ox}(W/L) = 500\mu A/V^2$.

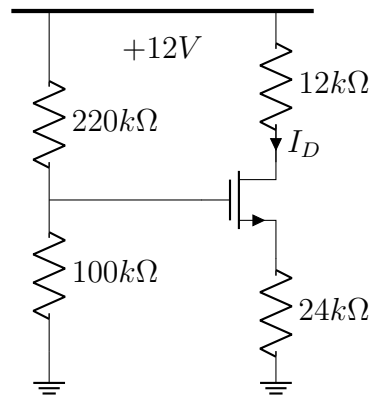


FIGURE 3. MOSFET circuit

Question 2. MOSFET DC Analysis I

Next, Xuyang assigns Christina the task of analyzing several simple circuits involving the MOSFET. For the circuits in Fig. 2, $V_{DD} = 3V$, $V_{TH} = 0.7V$ for NMOS, $V_{TH} = -0.8V$ for PMOS. She needs to sketch V_{out} as a function of V_{in} for each circuit as V_{in} varies from 0 to V_{DD} . Ignore body effect and channel length modulation.



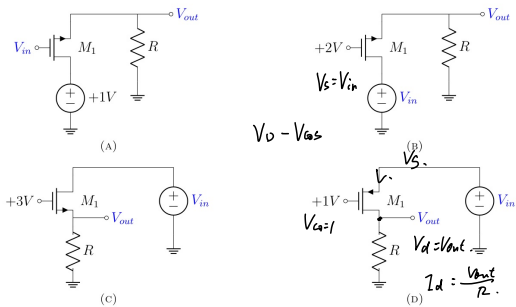
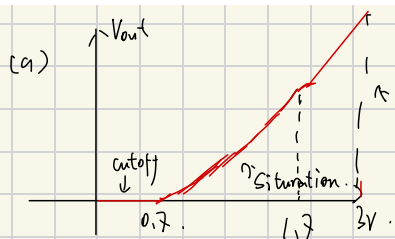



FIGURE 2. MOSFET circuits

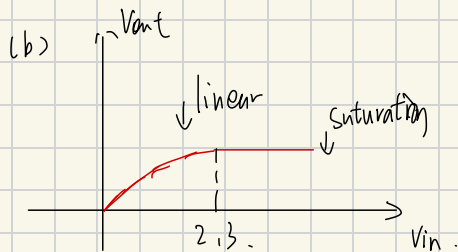
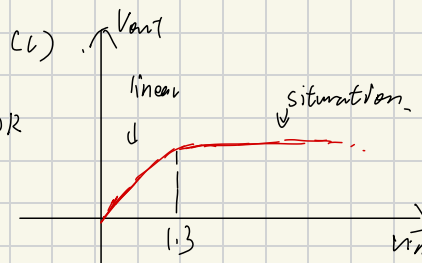
$$V_{in} = \begin{cases} 0-0.7V & \text{cutoff } V_{out}=0 \\ 0.7V-1.7V & \text{saturation } V_S = I_D R_1 = \frac{1}{2} k (V_G - V_{TH})^2 R_1 \\ 1.7V-3V & \text{linear } V_S = I_D R_1 = k R_1 (V_{GS}) \end{cases}$$



$$V_{in} = \begin{cases} 0-1.3V & \text{linear } V_S = I_D R_1 = k V_{GS} R_1 \\ 1.3V-3V & \text{saturation } V_S = I_D R_1 = \frac{1}{2} k (V_G - V_{TH})^2 R_1 \end{cases}$$

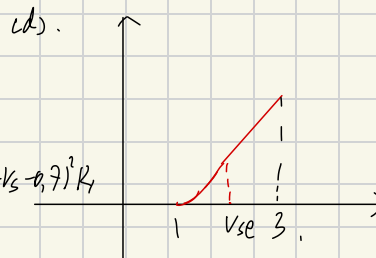

Question 3. MOSFET DC Analysis II

Then, Xuyang assigns Christina the task of finding DC bias current I_D through the NMOS transistor in Fig. 3. $V_{TH} = 1V$, $\lambda = 0$, $k_n = \mu_n C_{ox} (W/L) = 500 \mu A/V^2$.

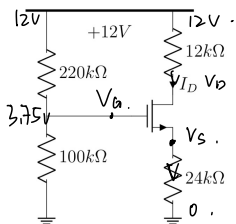


FIGURE 3. MOSFET circuit

$$V_{in} = \begin{cases} 0-1V & \text{cutoff} \\ 1V-V_{GS} & \text{saturation, } V_{out} = I_D R_1 = \frac{1}{2} k (V_G - V_{TH})^2 R_1 \\ V_{GS}-3V & \text{linear, } V_{out} = I_D R_1 = k V_S R_1 \text{ linear} \end{cases}$$

$$\begin{cases} I_D = \frac{V_S}{24 \times 10^3} \\ I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ V_{GS} = 3.75V \end{cases}$$

$$\frac{1}{2} \cdot 500 \times 10^{-6} (3.75 - V_S)^2 = \frac{V_S}{24 \times 10^3}$$

$$V_1 = 2.15V \quad V_2 = 3.51V$$

$$\text{Because } 3.75 - 1 - V_S > 0.$$

$$V_S = 2.15V$$

$$I_D = \frac{2.15}{24 \times 10^3} = 0.09 \times 10^{-3} = 9 \times 10^{-5} A$$

Question 4. MOSFET DC Analysis III

Finally, Xuyang assigns Christina the task of analyzing a complex circuit involving a combination of MOSFETs. For the circuit in Fig. 4, she needs to determine the labeled node voltages. The NMOS transistor has $V_{TH} = 0.9V$, $k_n = \mu_n C_{ox}(W/L) = 1.5mA/V^2$.

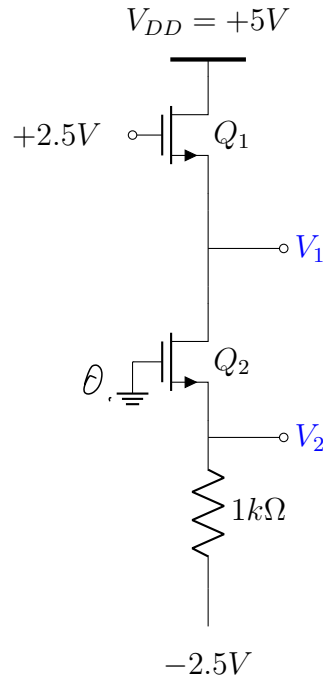


FIGURE 4. Two-MOSFET circuit

$$\begin{cases} \left(\frac{V_2 + 2.5}{10^5} \right) = \frac{1}{2} k_n (V_{GS1} - V_{TH})^2 & \left(\frac{-1.83 + 2.5}{10^5} \right) = \frac{1}{2} k_n (2.5 - V_1 - 0.9)^2 \\ \left(\frac{V_2 + 2.5}{10^5} \right) = \frac{1}{2} k_n (V_{GS2} - V_{TH2})^2 & V_{GS1} = 0.65 \quad V_{GS2} = 2.54 \\ & 2.5 - V_1 - 0.9 > 0 \\ & V_1 = 0.65V \end{cases}$$

$$\begin{aligned} \left(\frac{V_2 + 2.5}{10^5} \right) &= \frac{1}{2} k_n (0 - V_2 - 0.9)^2 \\ V_{GS1} &= 1.37 \quad V_{GS2} = -1.83 \\ 0 - V_2 - 0.9 &> 0 \\ V_2 &= -1.83V \end{aligned}$$