

---

UM-SJTU JOINT INSTITUTE

VE311

---

LABORATORY REPORT

EXCERCISE 2

Name: Shi Chengyang ID:523370910132 Group:Wed-3  
Date: August 7, 2025

[rev4.1]

# 1 Experiment Results

## 1.1 The Early Effect

In this section, we build the following circuit.

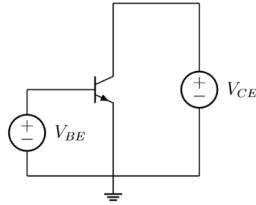


Figure 2: BJT Early Effect Voltage Measurement Circuit

Figure 1: Circuit

Then we have got the following result.

Table 1: Measured  $i_C$

	$V_{CE1}(1.2V)$	$V_{CE2}(2.2V)$	$V_{CE3}(2.8V)$	$V_{CE4}(3.4V)$	$V_{CE5}(4.1V)$	$V_{CE6}(5V)$
$V_{BE} = 0.7V$	0.033	0.068	0.093	0.117	0.142	0.168
$V_{BE} = 0.8V$	0.055	0.092	0.116	0.149	0.206	0.242

According to the formula

$$i_C = \frac{I_s V_{BE}}{V_T} \left( 1 + \frac{V_{CE}}{V_A} \right)$$

Then, plug in the data, we can plot the relationship between  $V_{CE}$  and  $i_C$

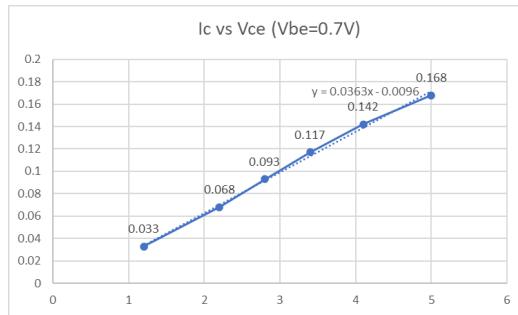


Figure 2:  $i_C$  VS  $V_{CE}$  ( $V_{BE} = 0.7V$ )

Then, we can calculate that  $V_A = \frac{3.012+3.781}{2} = 3.397V$

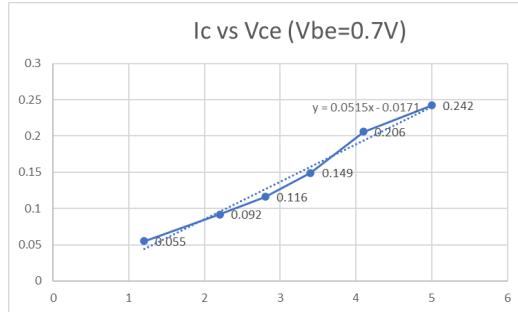


Figure 3:  $i_C$  VS  $V_{CE}$  ( $V_{BE} = 0.8V$ )

## 1.2 The Common-Emitter Amplifier

### 1.2.1

We can construct the following simulation circuit.

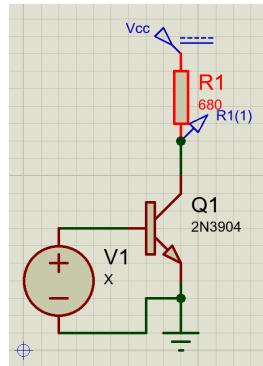


Figure 4: Simulation Circuit

Then, we can use DC Sweep to explore the relationship between  $V_{in}$  and  $V_{out}$ . From the figure, we can see that when  $V_{in} < 7.3V$ ,  $A_v = 80 > 10$ .



Figure 5: Simulation Result

When  $V_{in} > 7.3V$ , it reaches the saturation area.

### 1.2.2

In the lab, we have the measured data: According to our calculation,  $Av$

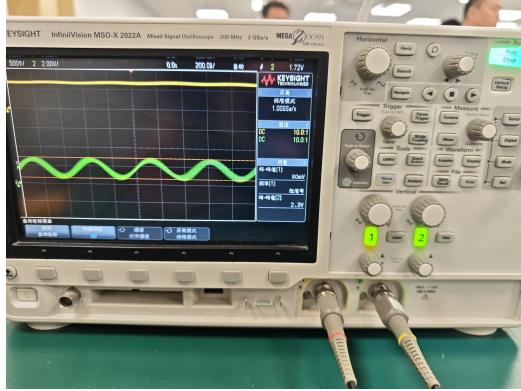


Figure 6: Measured data

should be equal to  $\frac{2.3}{0.02} = 115$ , which is close to 80, we can claim that our result is accurate.

### 1.3

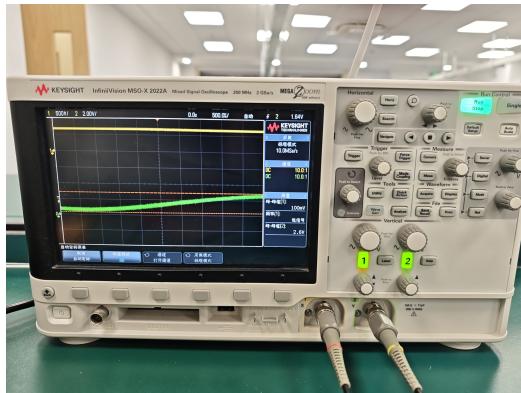


Figure 7: Measured Data

Similarly, we can calculate  $Av = \frac{2.6}{0.02} = 130$ , which is also close to 80, showing that our result is accurate.

## 2 Discussion

### 2.1 The Early Effect

The characterization of the Early Voltage ( $V_A$ ) for the 2N3904 BJT revealed the inherent sensitivity of this parameter. During the measurement process, which involved applying a constant  $V_{BE}$  while varying  $V_{CE}$ , any observed fluctuations in the collector current directly impact the graphically extrapolated value of  $V_A$ . These inconsistencies underscore the necessity of stable environmental conditions, as factors like temperature can alter the semiconductor's properties and, consequently, the measurement's stability and reliability.

### 2.2 The Common-Emitter Amplifier

The performance of the designed common-emitter amplifier is fundamentally limited by the intrinsic properties of the BJT, particularly at high frequencies. The design successfully achieved a voltage gain greater than 10 at a low frequency by selecting an appropriate bias point and load resistance ( $R_C$ ). At high frequencies, the impedance of these capacitances becomes minimal, effectively creating a shunt path for the signal, which bypasses the amplification mechanism and leads to a reduced output voltage amplitude.

## 3 Conclusion

In conclusion, we have explored some useful properties of BJTs in this lab, which helps me understand such electronic components better.