
UM-SJTU JOINT INSTITUTE

VE311

LABORATORY REPORT

EXCERCISE 1

Name: Shi Chengyang ID:523370910132 Group:Wed-3
Date: May 28, 2025

[rev4.1]

1 Voltage Regulator

1.1

In this part, we get the following result.

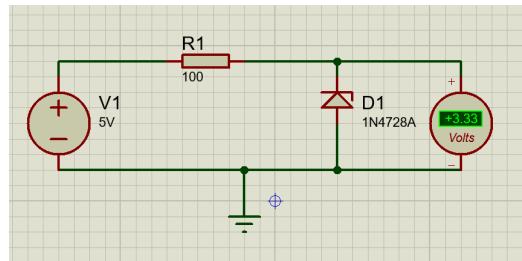


Figure 1: Simulation



Figure 2: Actual Result

The result we have got is $3.672V$, which is close to the theoretical result $3.3V$. Therefore, the result is reasonable.

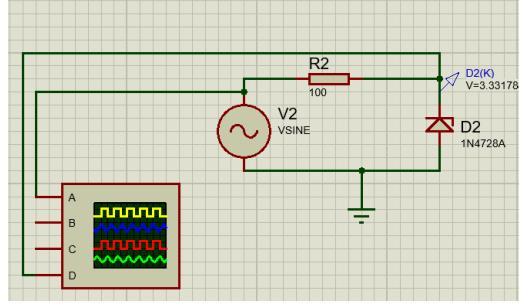


Figure 3: Simulation

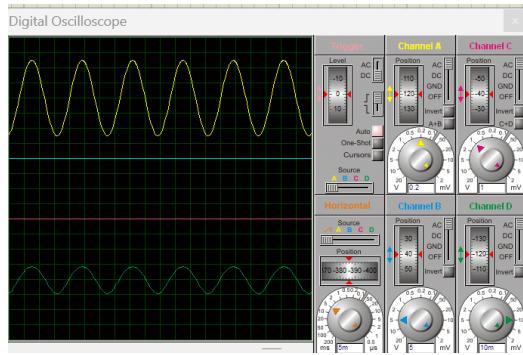


Figure 4: Oscilloscope

1.2

In our experiment, we have measured that $V_{spp} = 1.53V$, $V_{LPP} = 470mV$.

Accordingly, we can solve R_Z

$$\text{line regulation} = \frac{R_Z}{R + R_Z} = \frac{0.47}{1.53}$$

$$R_Z = 44.3\Omega$$

After changing the Voltage Source, we can get the following result.

1.3

In our experiment, when $R_L = 109.8V$, V_L reaches 2V and the diode stops working.

Based on the theoretical value, it will stop work when $R_L = 66.67V$. The error is a bit large due to the internal instrument bias or aging and the probe or connection issues.

If we want to make R_L two times smaller, R will be two times smaller accordingly.

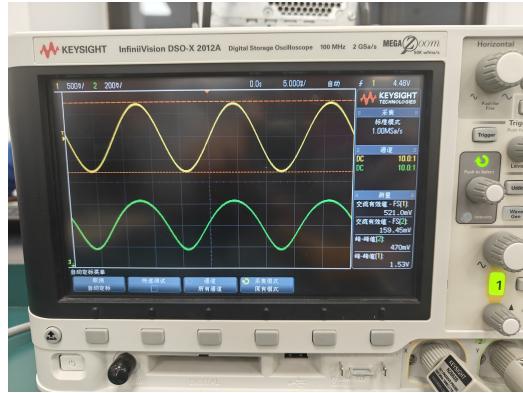


Figure 5: Result

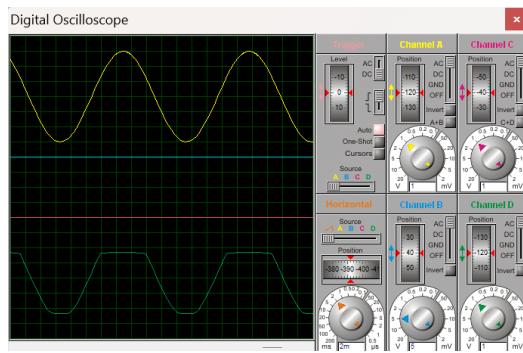


Figure 6: Simulation 2

2 Half-Wave Rectifier

In our experiment, we get the following result.

From the figure we can see that $V_r < 0.1V$, verifying our calculation.
Then, based on the simulation, we can calculate the corresponding value.



Figure 7: Result

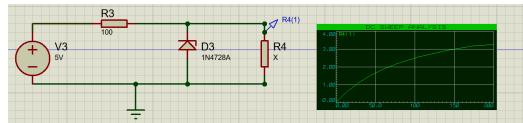


Figure 8: Simulation

$$V_r = (V_s - V_{on}) \left(\frac{T}{RC_{max}} \right)$$

$$C_{max} = 700 \mu F$$

$$V_{dc} = 5 - 0.8 = 4.2V$$

$$I_{dc} = \frac{V_{dc}}{R} = 4.2 \times 10^{-3} A$$

$$\theta_c = \sqrt{\frac{2V_r}{V_s}} = 0.2$$

$$\Delta T = \frac{\theta_c}{\omega} = 5.3 \times 10^{-4} s$$

$$I_{peak} = \frac{2I_{dc}T}{\Delta T} = 0.264 A$$

$$I_{surge} = \omega C V_s = 1.319 A$$

$$PIV = 2V_s - \frac{1}{2}V_r = 9.9V$$

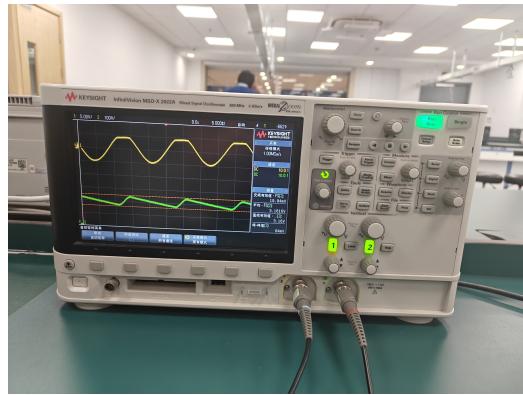


Figure 9: Result

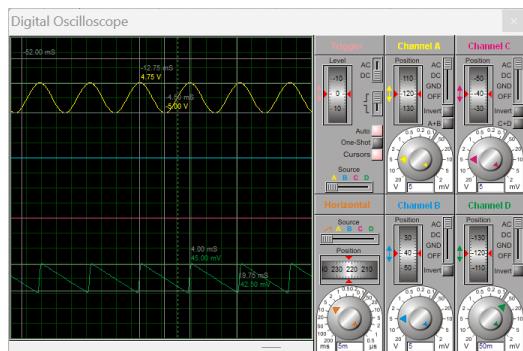


Figure 10: Simulation 1

If we change the frequency to 120Hz , V_r will be halved accordingly.

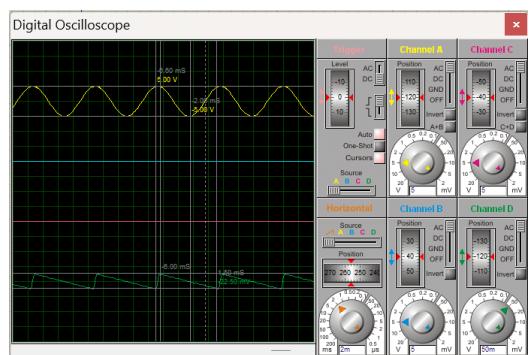


Figure 11: Simulation when $f = 120\text{Hz}$